

Fully-Integrated Power Management with Switched-Capacitor DC-DC Converters

Hanh-Phuc Le

Advisors: Prof. Elad Alon and Prof. Seth Sanders




UC Berkeley

Evolution of Chip Design

- Initially driven by number of transistors/chip
- More recently, driven by the performance (freq.)
- Today, power becomes an important part of the key drivers



from <http://vintagecomputerbits.com>

 

from <http://www.cobolhacker.com>



ITRS Roadmap 2009


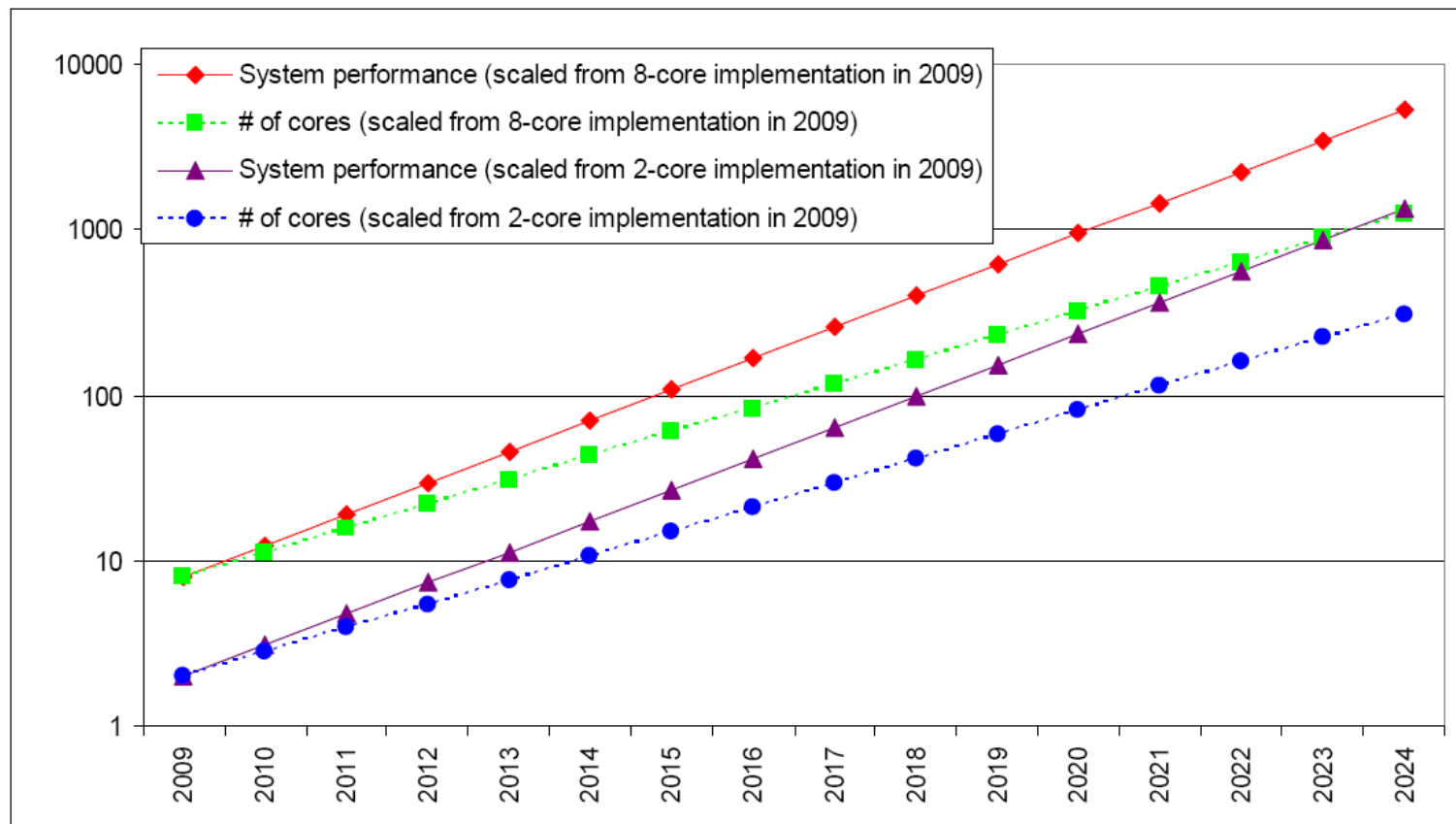
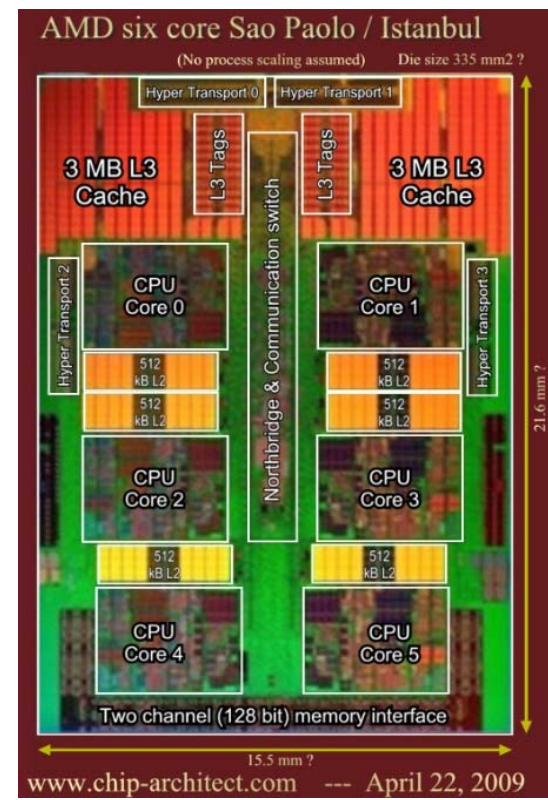


Figure SYSD2 SOC Networking Driver MC/AE Platform Performance

With constant die area:

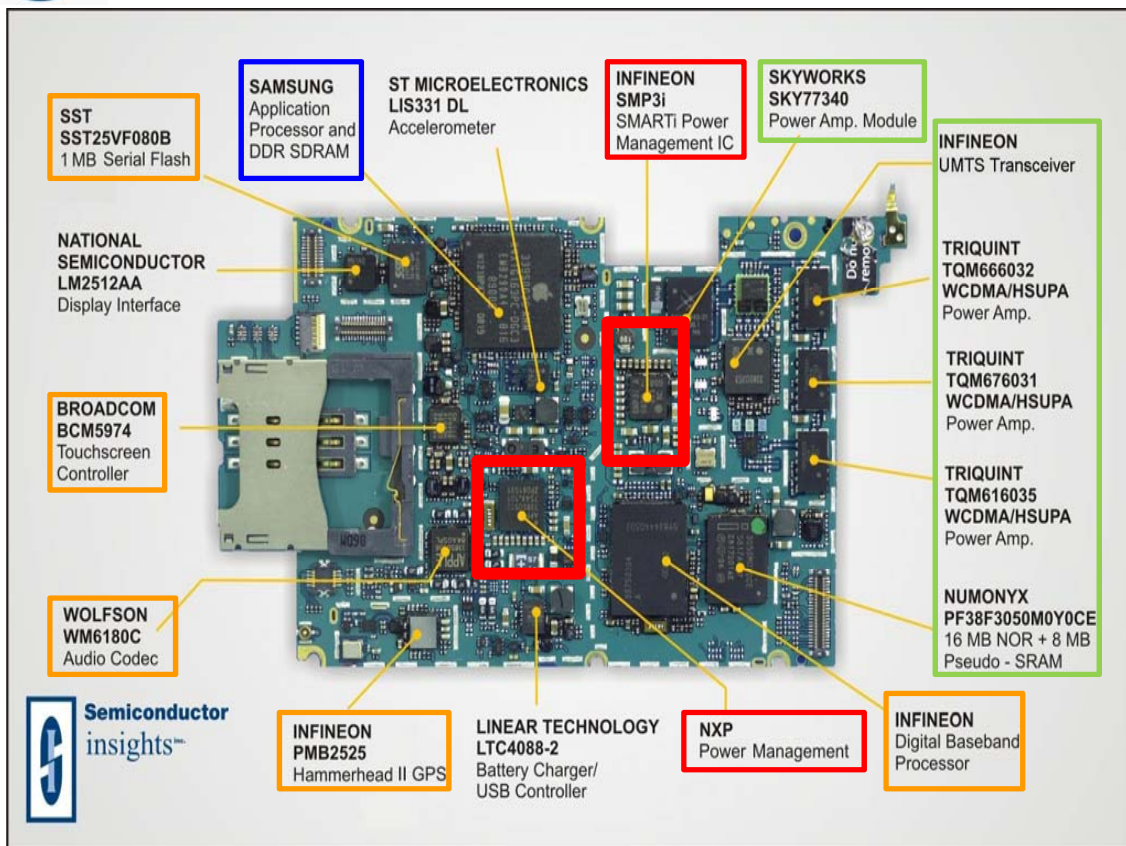- Core frequency increases by $1.05\times$ / year
- On-demand accelerator engine frequency increases by $1.05\times$ / year
- Number of cores increases by $1.4\times$ / year





- Integration has a benefit in energy efficiency

- Save IO power, board area


- Requirement?

- Need different voltage supply for different blocks/IPs and different modes of operations (DVS).

Limited Resources !

  

Power pins

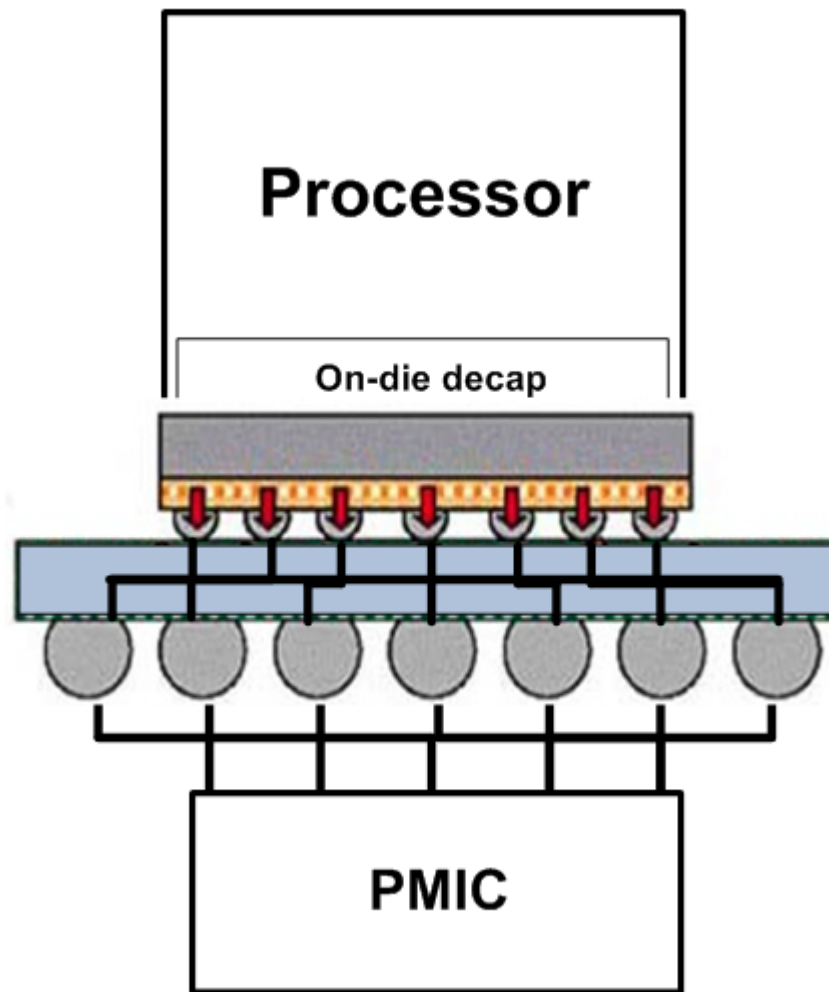


- But the resources (pins and decap) are limited




Multiple Off-chip Supplies: Not Appealing



 - Split power plane leads to supply impedance degradation
 - Compensating by de-cap is area-consuming → costly solution
- Just supplying power from off-chip is not appealing



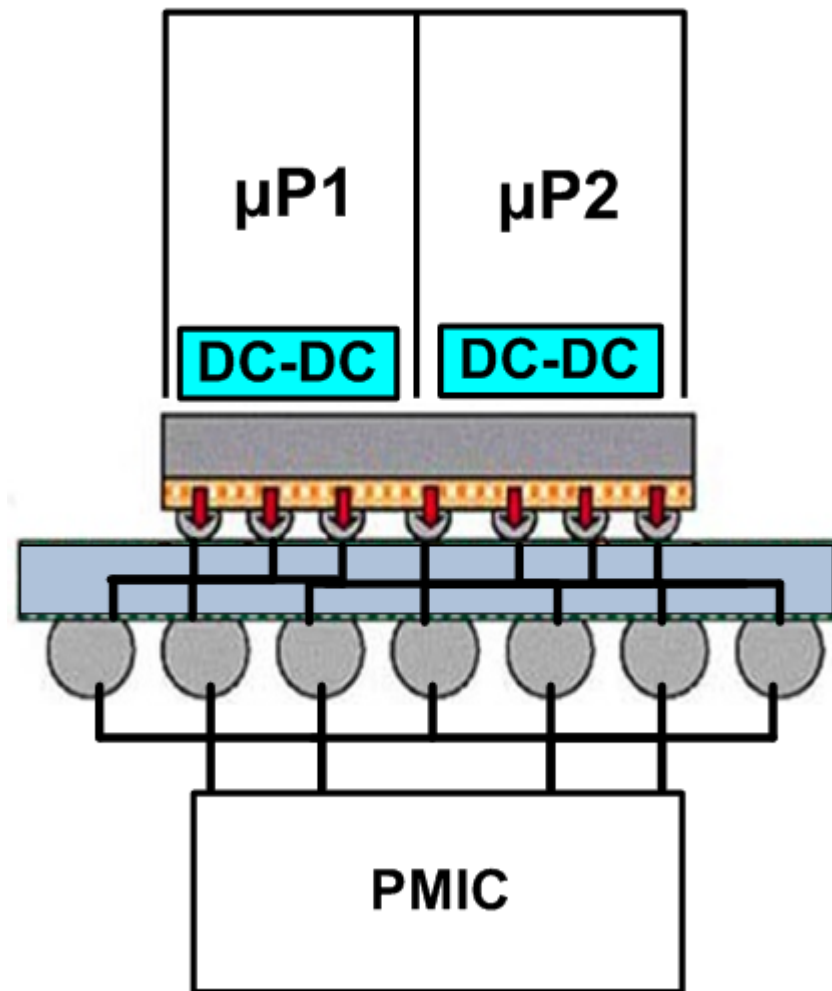- **One global supply onto die**
 - Local power generated by fully integrated DC-DC converters
- **Don't lose anything from package side**



→ How to make integrated DC-DC conversion efficient?



Outline



- Motivation

- Integrated converter efficiency
 - Choice of energy storage element
 - Why switched-capacitor
 - Efficiency analysis


- Switched-capacitor converter design and prototype



DC-DC Converter: Linear vs. Switching




Linear Regulator

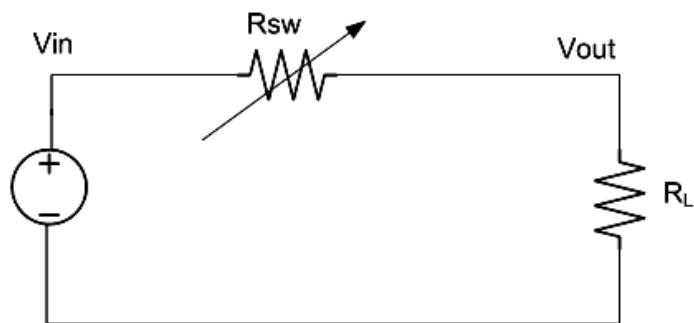

$$\eta = \frac{V_{out}}{V_{in}}$$

- Fundamental limit on efficiency


Switching Regulator

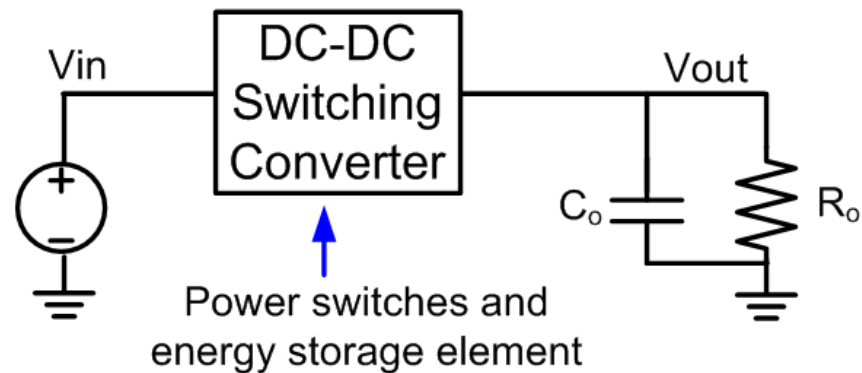

Inductor or Capacitor?

- Efficiency is ideally independent of conversion ratio.
- Theoretically, can reach up to 100% efficiency


Phase 1

 

- Two-phase operation

- Phase 1: charge capacitor



Phase 2

 

- Phase 2: capacitor transfers charge to output



First Look at Switch Utilization

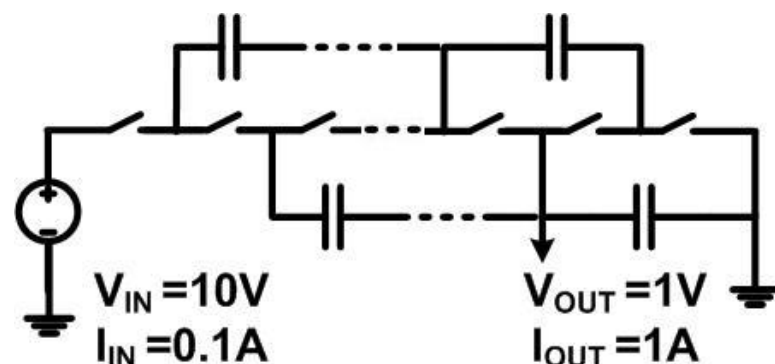 

Magnetic boost/buck:

- 10-to-1 V conversion, 1A @ 1V
- S1,S2 rated for V-A product of
 - $V \cdot I = 10 \text{ V-A}$
- Sum up to 20 V-A


→ Require high voltage switches

10-to-1 Ladder Switched-Cap:

- 10-to-1 V conversion, 1A@1V
- 20 switches, each blocks 1V
 - 18 switches handle $1/5 \text{ A}$
 - 2 switches handle $9/5 \text{ A}$
- V-A product sums up to $36/5 = 7.2 \text{ V-A}$

→ Native CMOS device convenient


Inductor

 

- Very popular for a wide range of off-chip applications

- Standard CMOS inductors have high series resistance → low efficiency
- **Technology modifications are costly**

Capacitor

 

- Usually considered appropriate for “low power”


- High Q, high capacitance density.
- **Highly compatible with commercial CMOS process**



Switched Capacitor Power Converters



 - **Only switches and capacitors**
- **Using no inductors has advantages:**
 - Simplified full integration potential
 - Works well over a wide power range
 - Single mode, can adjust clock rate
 - No minimum load
 - No inductive switching losses





Why Not S-C ?





- Voltage rating of CMOS processes?
- Not suited for high current/power?
 - Magnetic-based ckts = higher performance?
- Ripple?
- Interconnect difficulty for many caps?
- Difficult regulation?




Previous Work

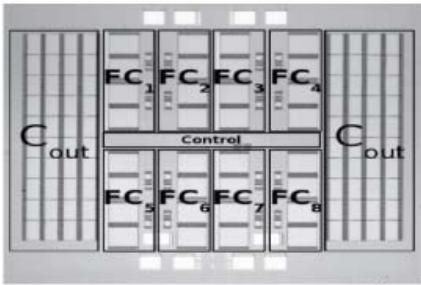

Work	[1] Breussegem, VLSI 09	[2] Somasekhar, VLSI 09
Technology	130nm Bulk	32nm Bulk
Topology	2/1 step-up	2/1 step-up
Interleaved Phases	16	32
Converter Area (mm ²)	2.25	6.678x10 ⁻³
Power density @ η_{\max}	2.09 mW/mm ²	1.123 W/mm ²
Efficiency (η_{\max})	82%	60%
Die photo		

Switched Capacitor Loss

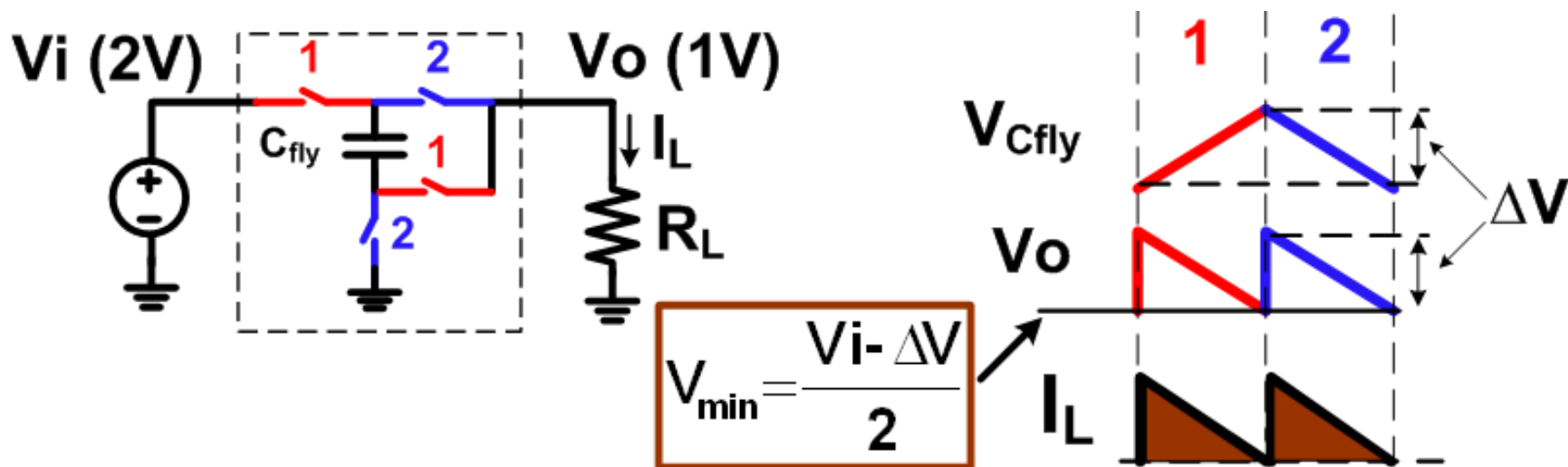




- **Converter supplies digital circuits**
 - Performance (f_{CPU}) set by V_{min}

- **Intrinsic switched-capacitor loss:**


$$P_{C_{fly}} = 2x \frac{I_L^2}{M_{conv,cap} f_{sw} C_{fly}}$$



Multi-Phase Interleaving

   

 Maximum Efficiency vs. Interleave
($V_{in}=2V$, $br=2.7\%$)





▪ **Good news:**

- Interleaving can reduce ripple without changing V_{min}

$$P_{C_{fly}} = \left(1 + \frac{1}{k_{interleave}} \right) \frac{I_L^2}{M_{conv,cap} f_{sw} C_{fly}}$$

SC – Loss Optimization

  

• 4 main loss components

$$P_{loss} = P_{R_{sw}} + P_{C_{fly}} + P_{bott.cap} + P_{gate.cap}$$

$\propto I_L^2 \frac{R_{on}}{W_{sw}}$

Switch resist.

$\propto \frac{I_L^2}{f_{sw} C_{fly}}$

Switched cap

$\propto C_{bott} f_{sw}$

Bottom Plate

$\propto W_{sw} C_{gate} f_{sw}$



Gate loss

Series Losses (R_o)

Parasitic Losses ($R_{//}$)



Optimization for Efficiency

 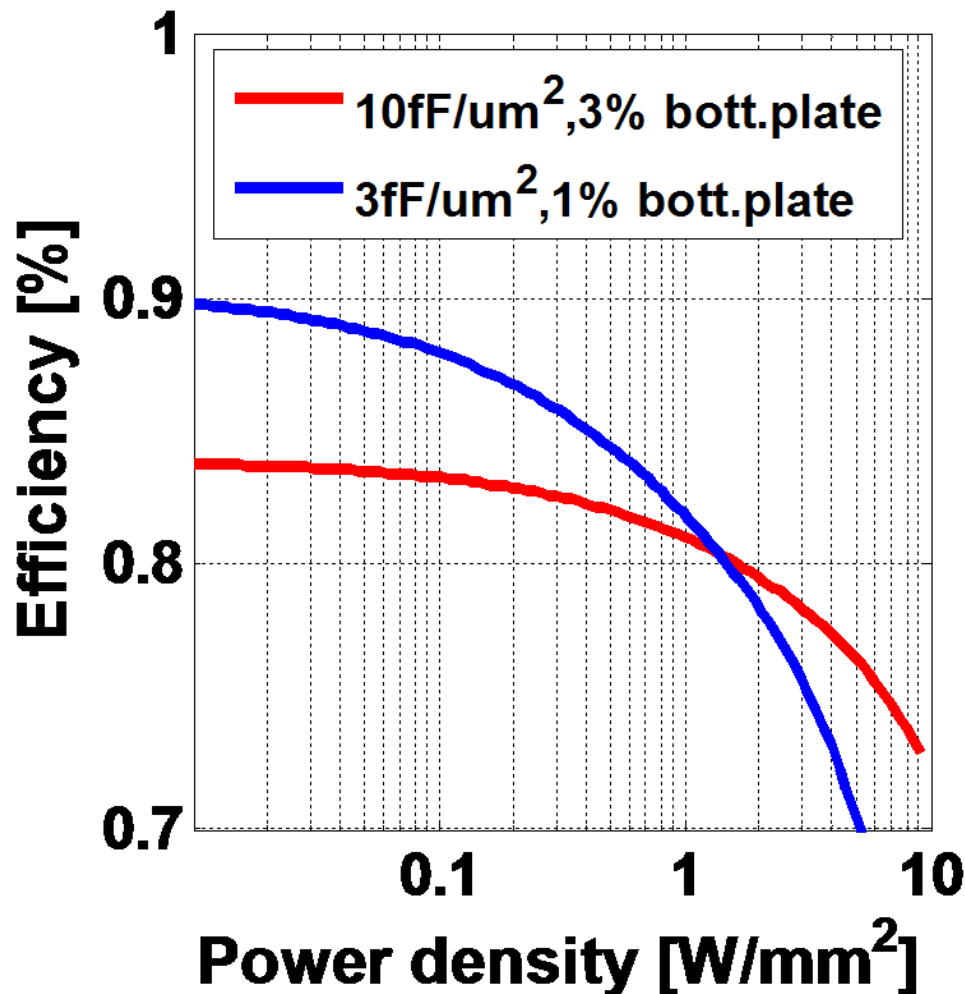

- Efficiency trades off with power density
- Low power density:
 - Bottom plate critical
- High power density:
 - Flying cap critical

$$\frac{P_{\text{loss}}}{P_{\text{Load}}} \approx \sqrt{M_{\text{conv}} k_{\text{bott}}} + \sqrt{\frac{1}{\sqrt{M_{\text{conv}} k_{\text{bott}}}}} \frac{V_{\text{sw}}^2 R_{\text{on}} C_{\text{sw}}}{V_o^2 R_L C_{\text{fly}}}$$




Achievable Performance



- **Looks promising**
 - Especially in mobile applications
 - 1W/mm² converter fits in decap area
- **Only looked at 2:1 converter so far**
 - Need to support multiple output voltage levels

Eff. vs. Cap Density

($k_{\text{bott}} = 3\%$)

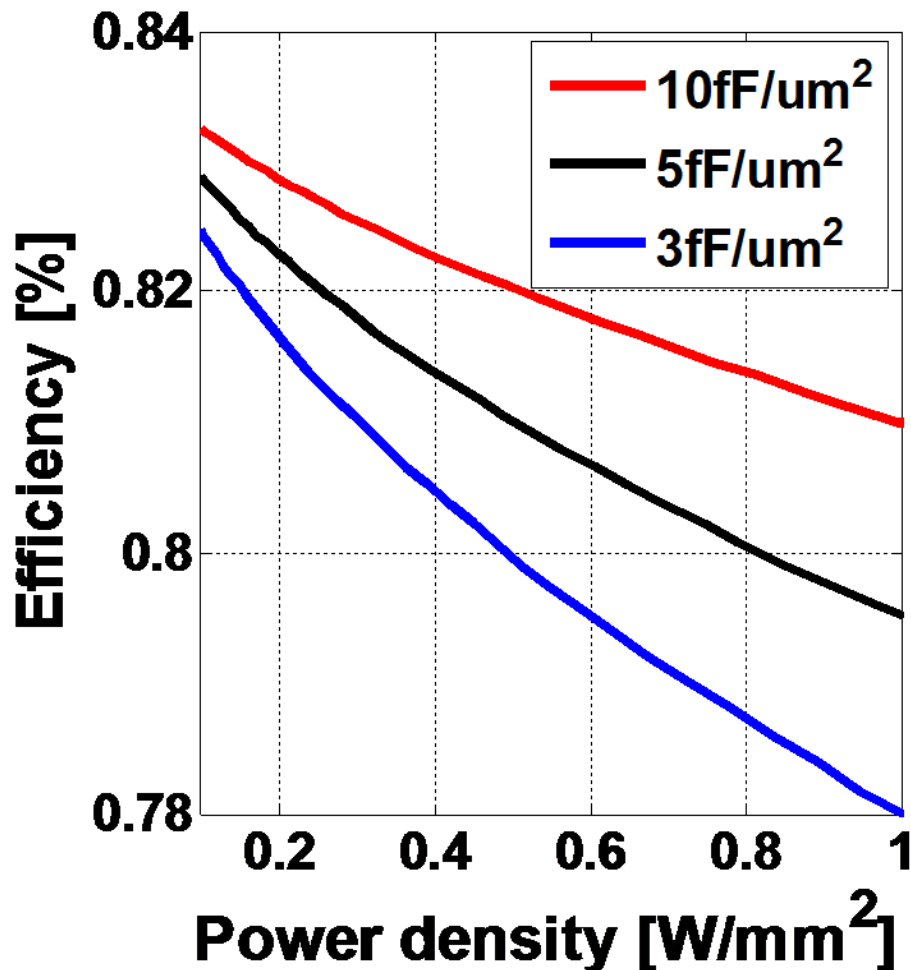



Outline







- Motivation

- Integrated converter efficiency
 - Choice of energy storage element
 - Why switched-capacitor
 - Efficiency analysis


- Switched-capacitor converter design and prototype





Multiple Conversion Ratios

    

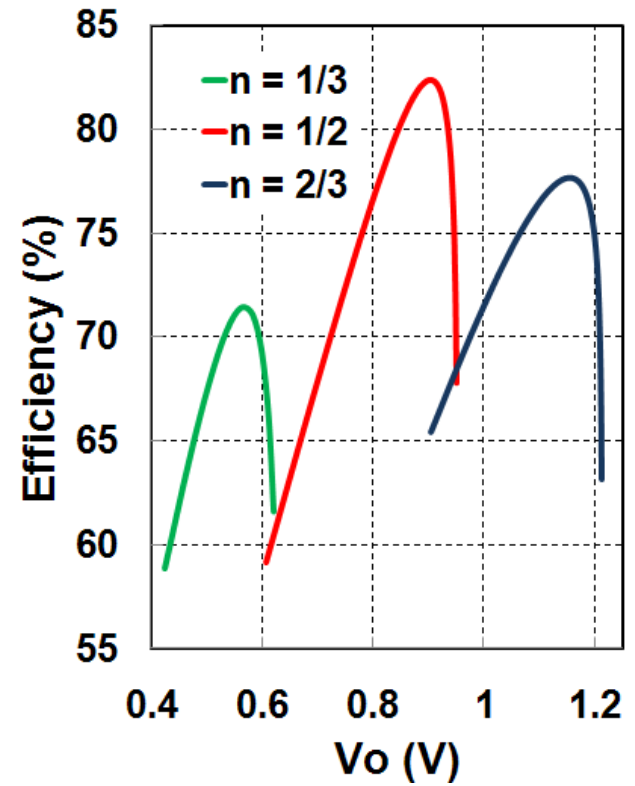- **Standard cell design supports multiple conversion ratios**
- **Fine output voltages achieved by controlling f_{sw} (or W_{sw})**
 - Equivalent to linearly regulating down from peak efficiency
- **How to drive the switches?**



Switch Drivers


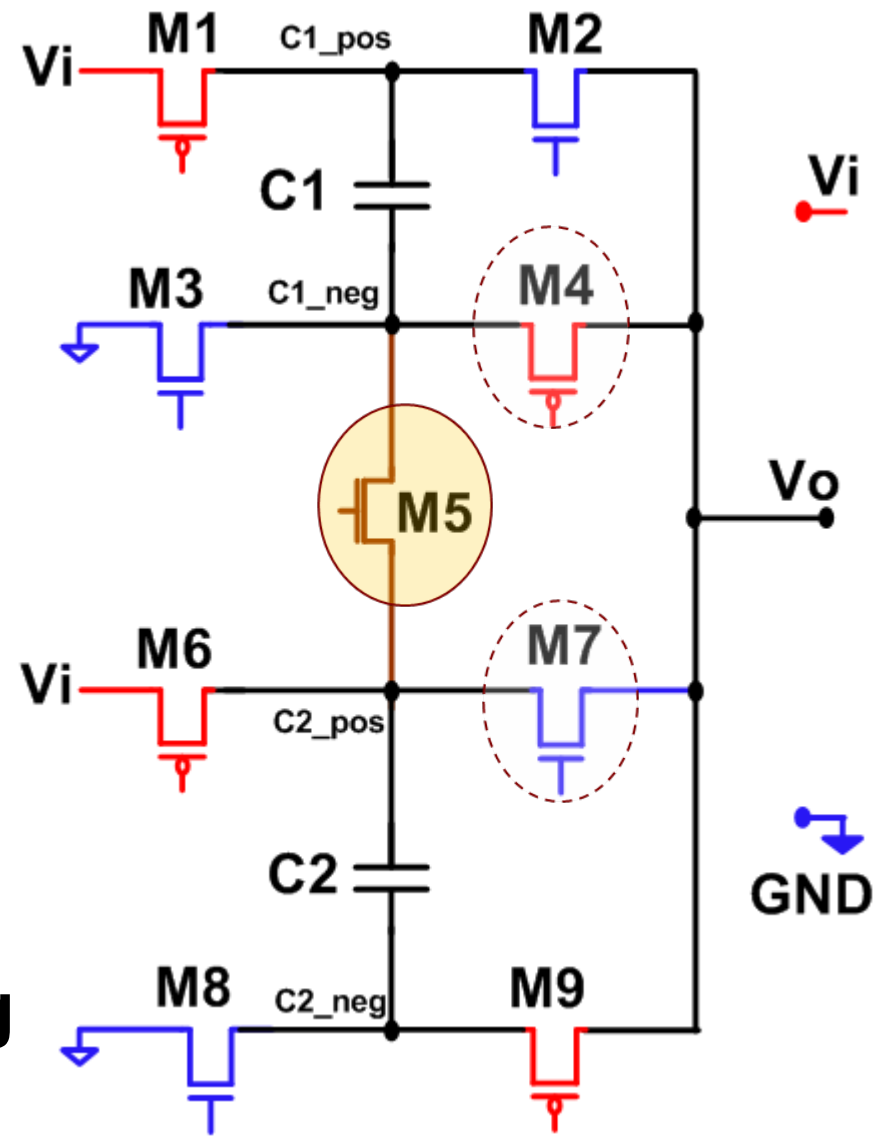
 


- **Most switches easy to drive**
 - 2 voltage domains:
 - $(V_i - V_o)$
 - $(V_o - GND)$

- **M4, M5, and M7 challenging**
 - Experience voltages between the two domains




Switch Driver – M5

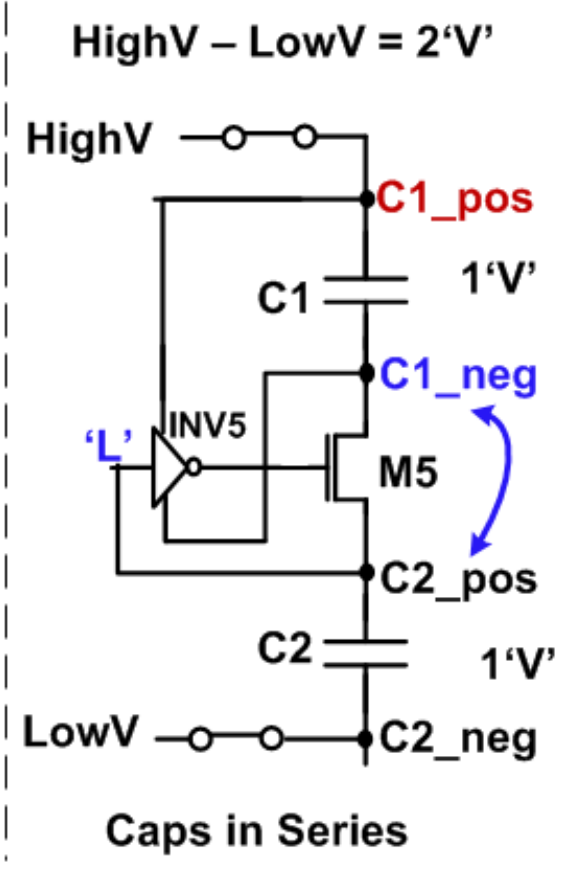
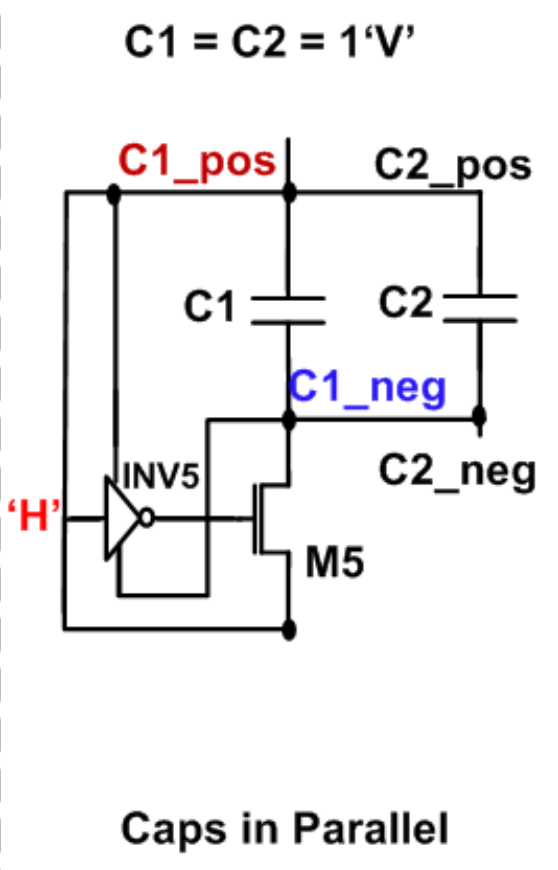
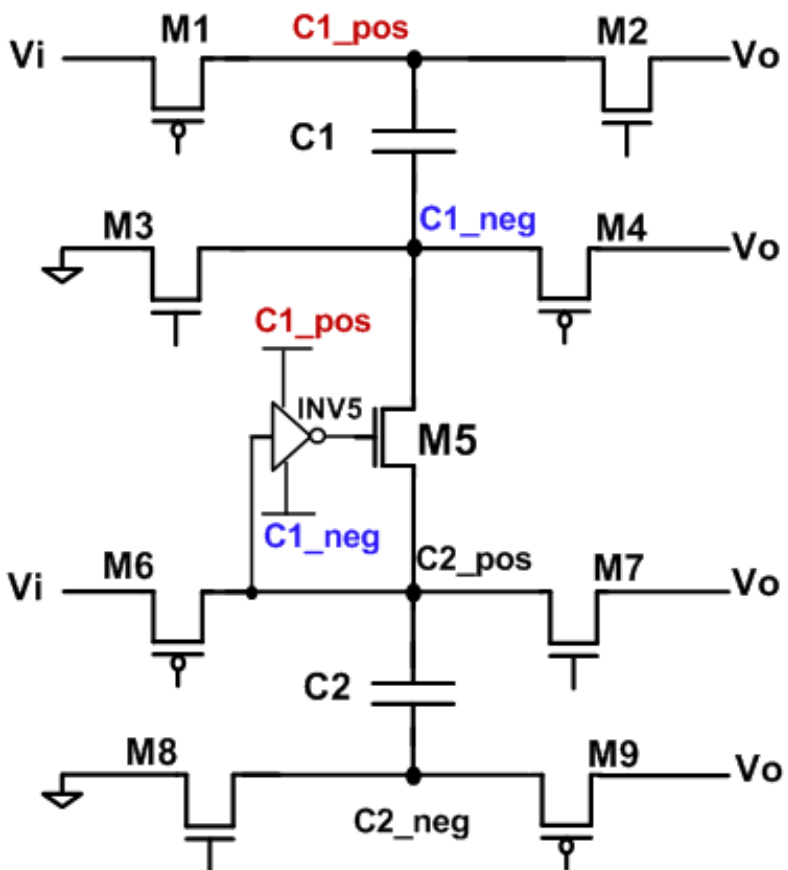


- “Flying” inverter INV5 powered off of C1
 - Controlled by top-plate of C2
- Automatically synchronized by operation of other switches

SC Converter Prototype


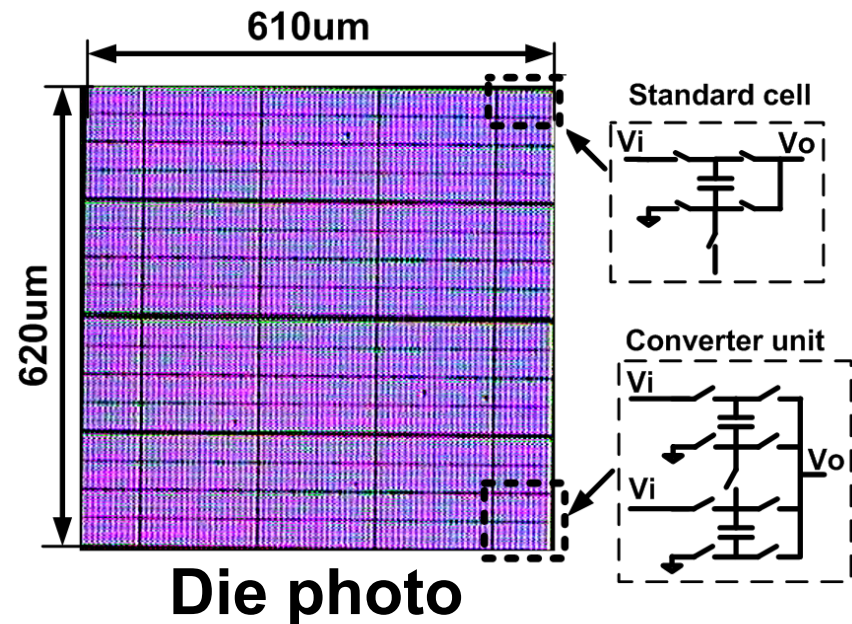


   - Implemented in 32nm SOI test-chip
- Flying cap: MOS, 32-way interleaved
- Supports 0.6V ~ 1.2V from 2V input





Measured Eff. vs. P-density

 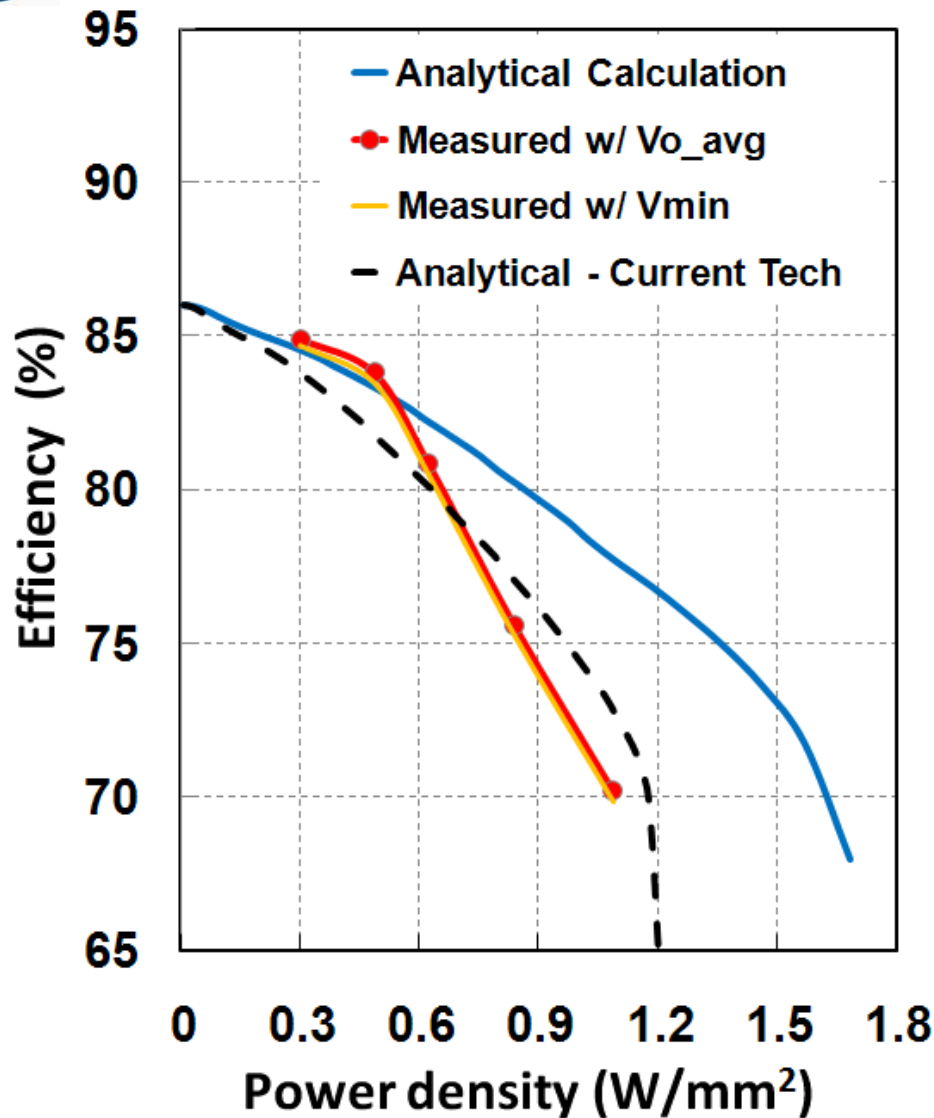


- Measured in 1/2 mode ($V_i = 2V$, $V_o \approx 0.88V$)
- Results promising: 82% efficiency @ 0.55 W/mm²




Measured Eff. vs. Topologies



Efficiency vs. V_o

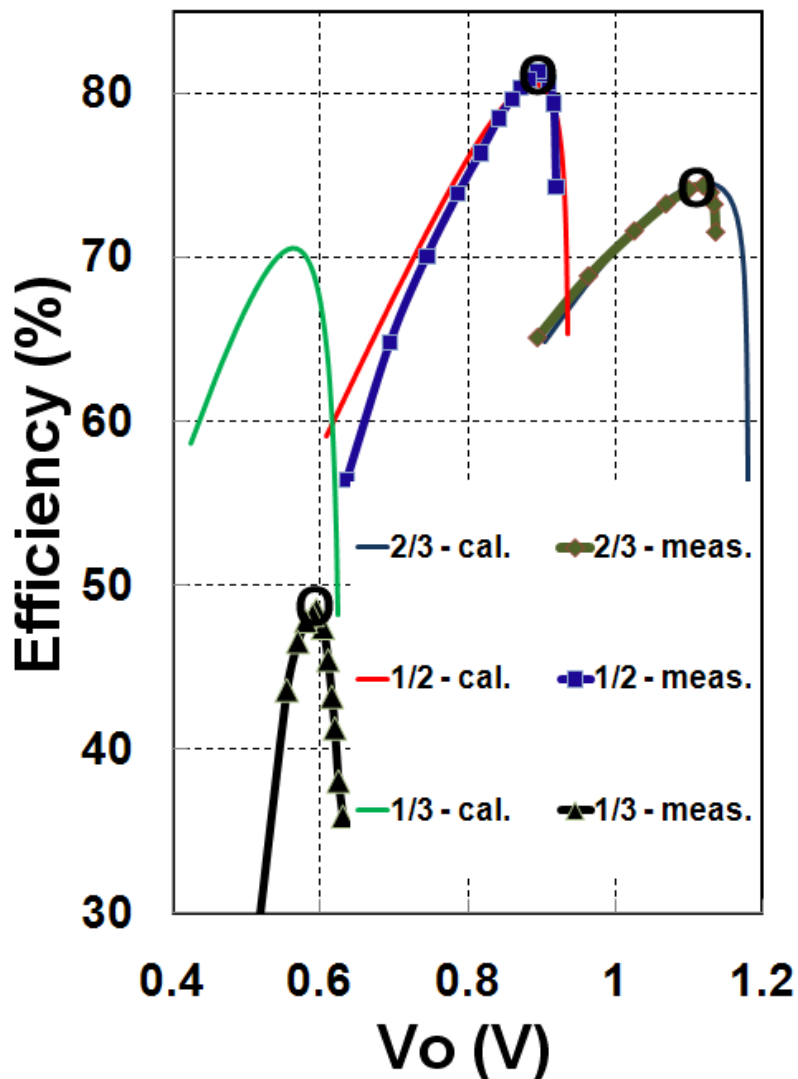

f_{sw} vs. V_o

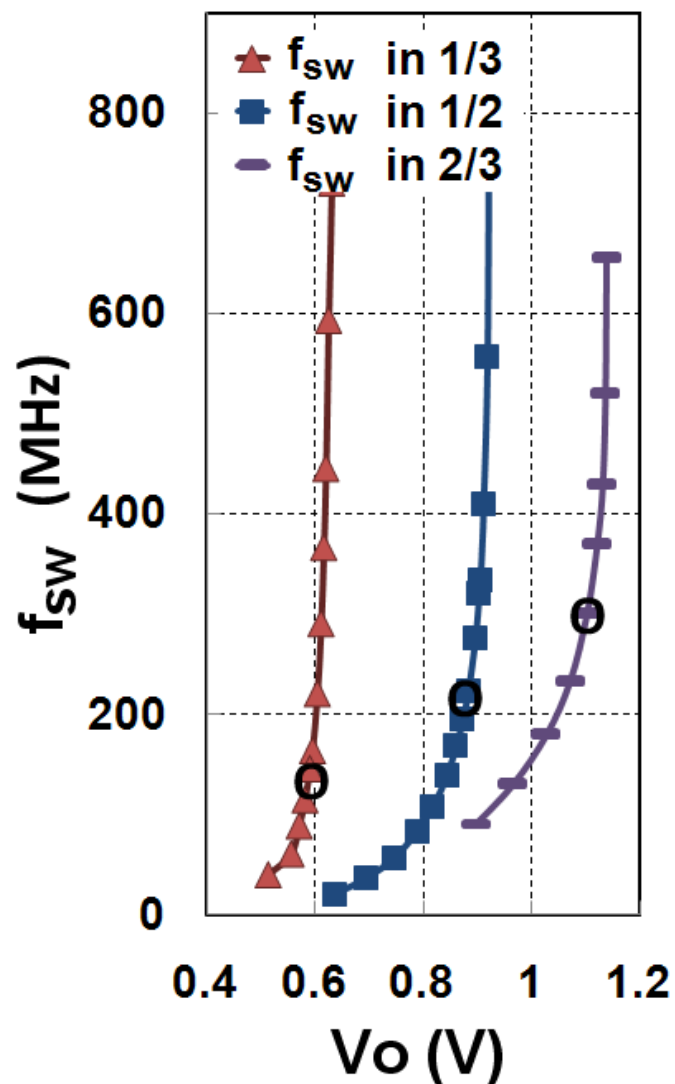

Settings:

$V_i = 2V$




$R_L \approx 4\Omega$ at

$V_o = 0.8V$



Previous Work

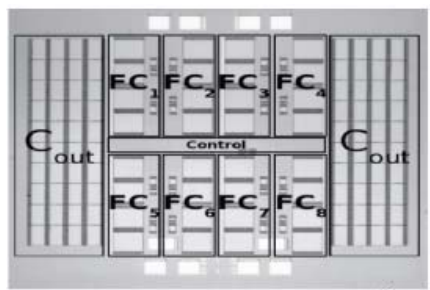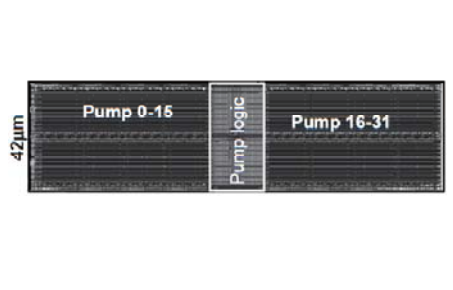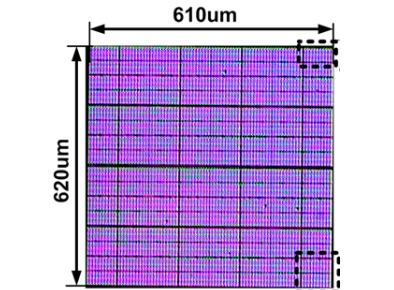

Work	[1] Breussegem, VLSI 09	[2] Somasekhar, VLSI 09	This work
Technology	130nm Bulk	32nm Bulk	32nm SOI
Topology	2/1 step-up	2/1 step-up	step-down 1/2, 2/3, 1/3
Interleaved Phases	16	32	32
Converter Area (mm ²)	2.25	6.678x10 ⁻³	0.36
Power density @ η_{\max}	2.09 mW/mm ²	1.123 W/mm ²	0.55 W/mm ²
Efficiency (η_{\max})	82%	60%	82%
Die photo			



Conclusions

- **Clear need for fully-integrated DC-DC converters**
 - Switched–capacitor converters a promising option
- **Design optimization enables both high power density and high efficiency**
 - In 2:1: 82% efficiency at $0.55\text{W}/\text{mm}^2$
- **Reconfiguration supports wide output voltage range**
 - $>70\%$ efficiency for V_o from $\sim 0.75\text{V}$ to 1.15V with $V_{in} = 2\text{V}$



Why Not S-C ?



- √ Voltage rating of CMOS processes?
- √ Not suited for high current/power?
 - Magnetic-based ckts = higher performance?
- √ Ripple?
- √ Interconnect difficulty for many caps?
- √ Difficult regulation?